

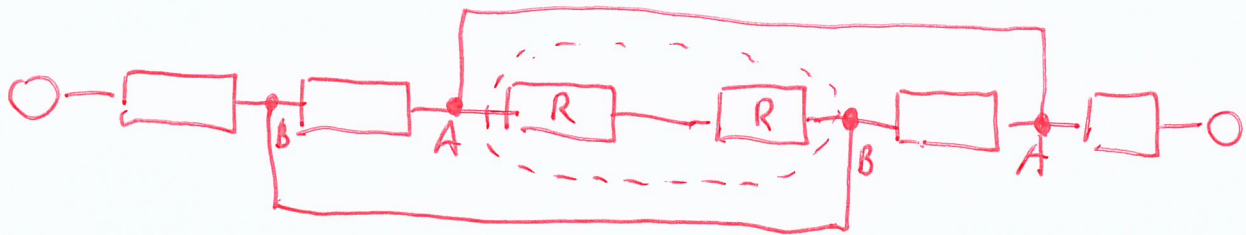



Zadanie 1

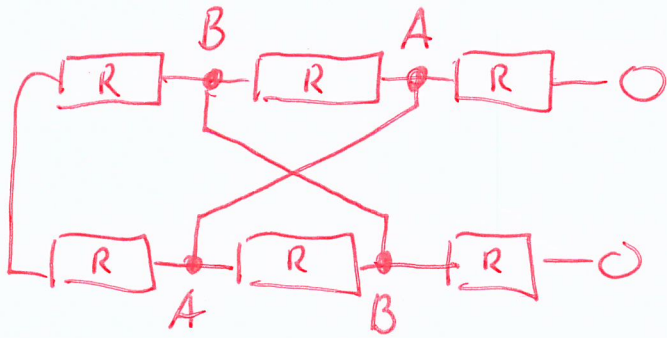


$$R_2 = R + R = 2R$$

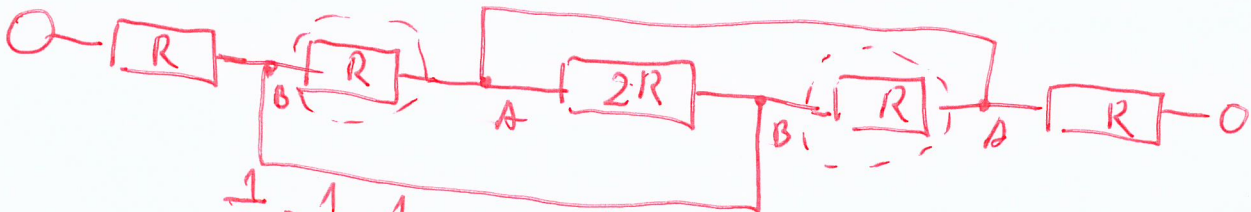
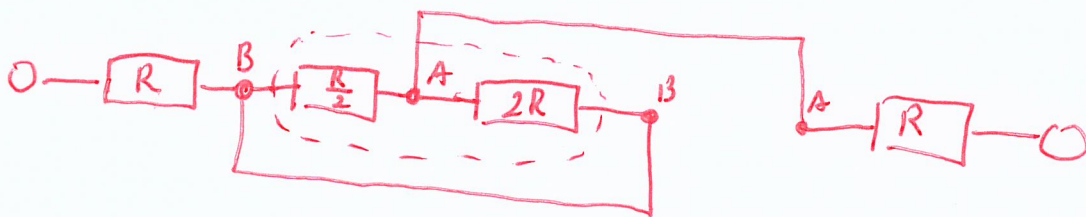
$$\frac{1}{R_2} = \frac{1}{R} + \frac{1}{R} \Rightarrow R_2 = \frac{R}{2}$$



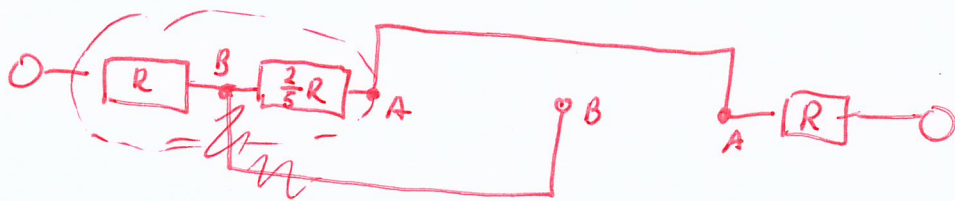
$$\frac{1}{R_2} = \frac{2}{R} + \frac{1}{2R} = \frac{4}{2R} + \frac{1}{2R} = \frac{5}{2R} \Rightarrow R_2 = \frac{2}{5}R$$



$$R_2 = 2\frac{2}{5}R$$

Zadanie 2

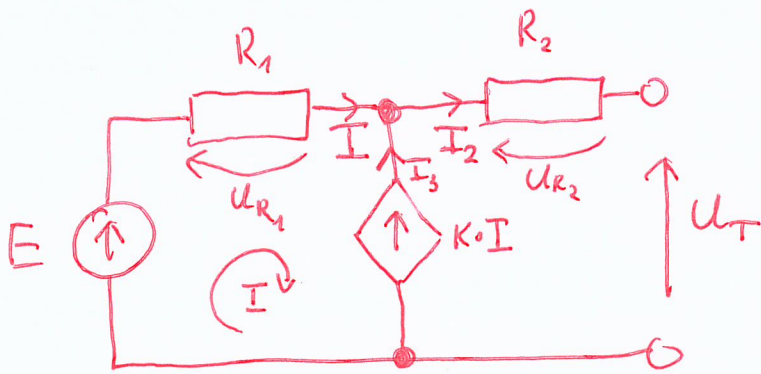

$$E - U_{R1} - K \cdot I = 0 \Rightarrow E - R_1 \cdot I - K \cdot I = 0$$

$$E = R_1 I + K \cdot I$$

$$E = I(R_1 + K)$$


$$\frac{E}{R_1 + K} = I$$

$$I_2 = 0$$

$$I = -I_3$$

$$U_T = K \cdot I$$

$$U_T = \frac{K}{R_1 + K} E$$

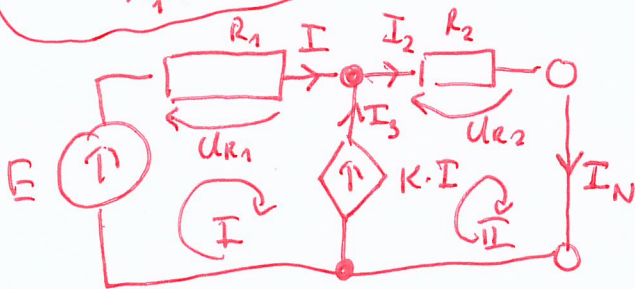

$$E - U_{R1} - K \cdot I = 0 \Rightarrow I = \frac{E}{R_1 + K}$$

$$I + I_3 = I_2$$

$$K \cdot I - U_{R2} = 0$$

$$I_2 = I_N$$

$$\frac{K}{R_1 + K} \cdot E - I_2 \cdot R_2 = 0 \Rightarrow \frac{K}{R_1 + K} \cdot E = I_2 \cdot R_2$$


$$\frac{K}{R_1 + K} \cdot \frac{1}{R_2} \cdot E = I_2 = I_N$$

$$R_T = \frac{U_T}{I_N}$$

$$R_T = \frac{\frac{K}{R_1 + K} \cdot E}{\frac{(R_1 + K) \cdot R_2}{K \cdot E}}$$

$$R_T = R_2$$

Zadanie 3

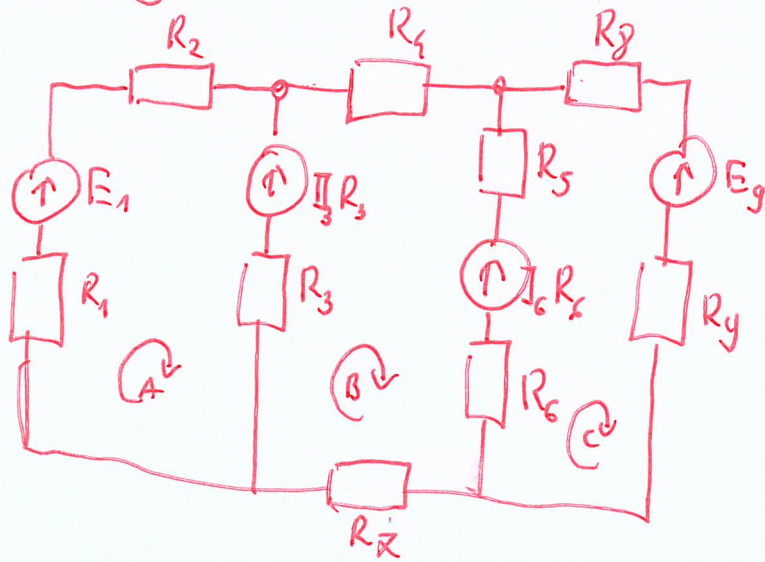


$$\begin{bmatrix} R_1 + R_2 + R_3 & -R_3 & 0 \\ -R_3 & R_3 + R_4 + R_5 + R_6 + R_8 & -R_5 - R_6 \\ 0 & -R_5 - R_6 & R_5 + R_6 + R_7 + R_9 \end{bmatrix} \begin{bmatrix} I_A \\ I_B \\ I_C \end{bmatrix} = \begin{bmatrix} E_1 - J_3 R_3 \\ J_3 R_3 - J_6 R_6 \\ J_6 R_6 - E_9 \end{bmatrix}$$

$$\begin{bmatrix} 1+1+2 & -2 & 0 \\ -2 & 2+2+1+1+1 & -1-1 \\ 0 & -1-1 & 1+1+1+1 \end{bmatrix} \begin{bmatrix} I_A \\ I_B \\ I_C \end{bmatrix} = \begin{bmatrix} 2 - 0.5 \cdot 2 \\ 0.5 \cdot 2 - 2 \cdot 1 \\ 2 \cdot 1 - 1 \end{bmatrix}$$

$$\begin{bmatrix} 4 & -2 & 0 \\ -2 & 7 & -2 \\ 0 & -2 & 4 \end{bmatrix} \begin{bmatrix} I_A \\ I_B \\ I_C \end{bmatrix} = \begin{bmatrix} 1 \\ -1 \\ 1 \end{bmatrix}$$

Zadanie 4

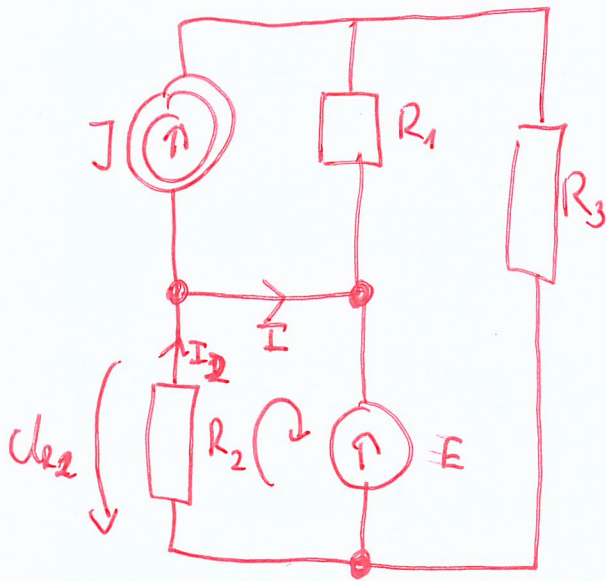

$$-U_{R_2} - E = 0$$

$$-R_2 \cdot I_2 = E$$

$$I_2 = -\frac{E}{R_2}$$

$$I + J = I_2$$

$$I = I_2 - J$$

$$I = -\frac{E}{R_2} - J$$